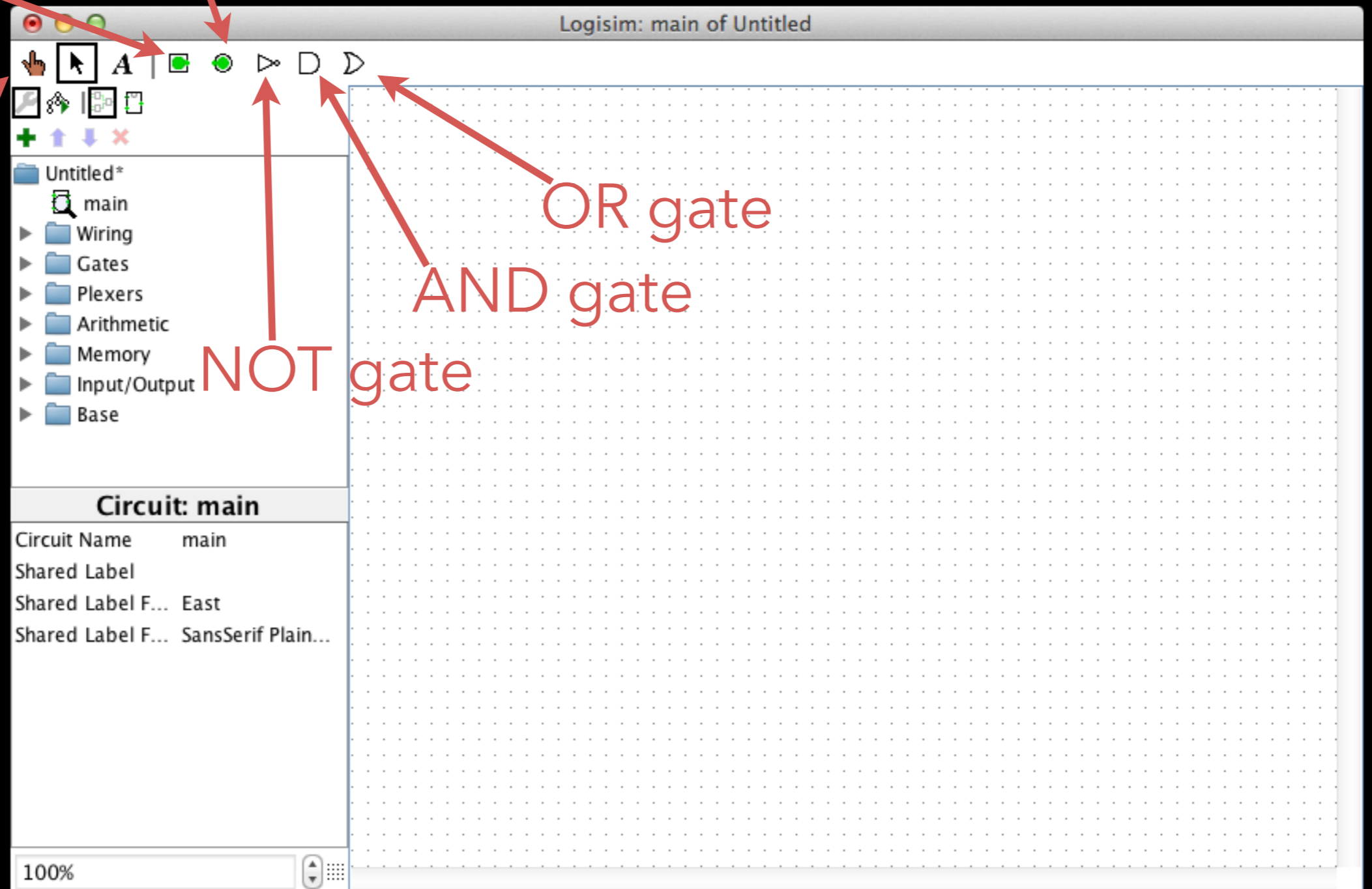


Meet Logisim

input tool

output tool

poke tool




Add a gate

Click on the AND gate

Click on the workspace to place it

Set the number of inputs to 2

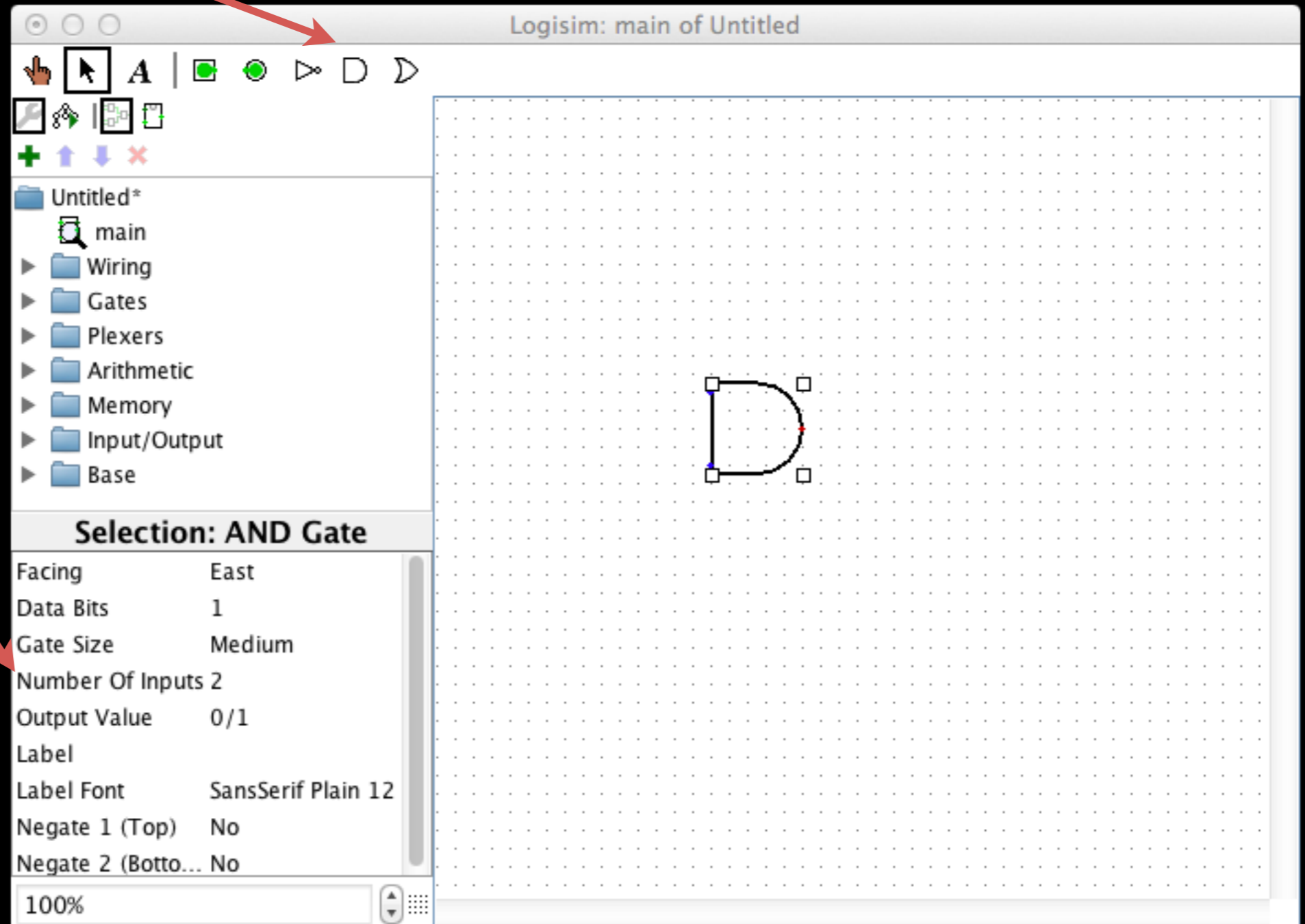


Connect the gate to some pins

Add two input pins behind the gate

Add an output pin in front of the gate

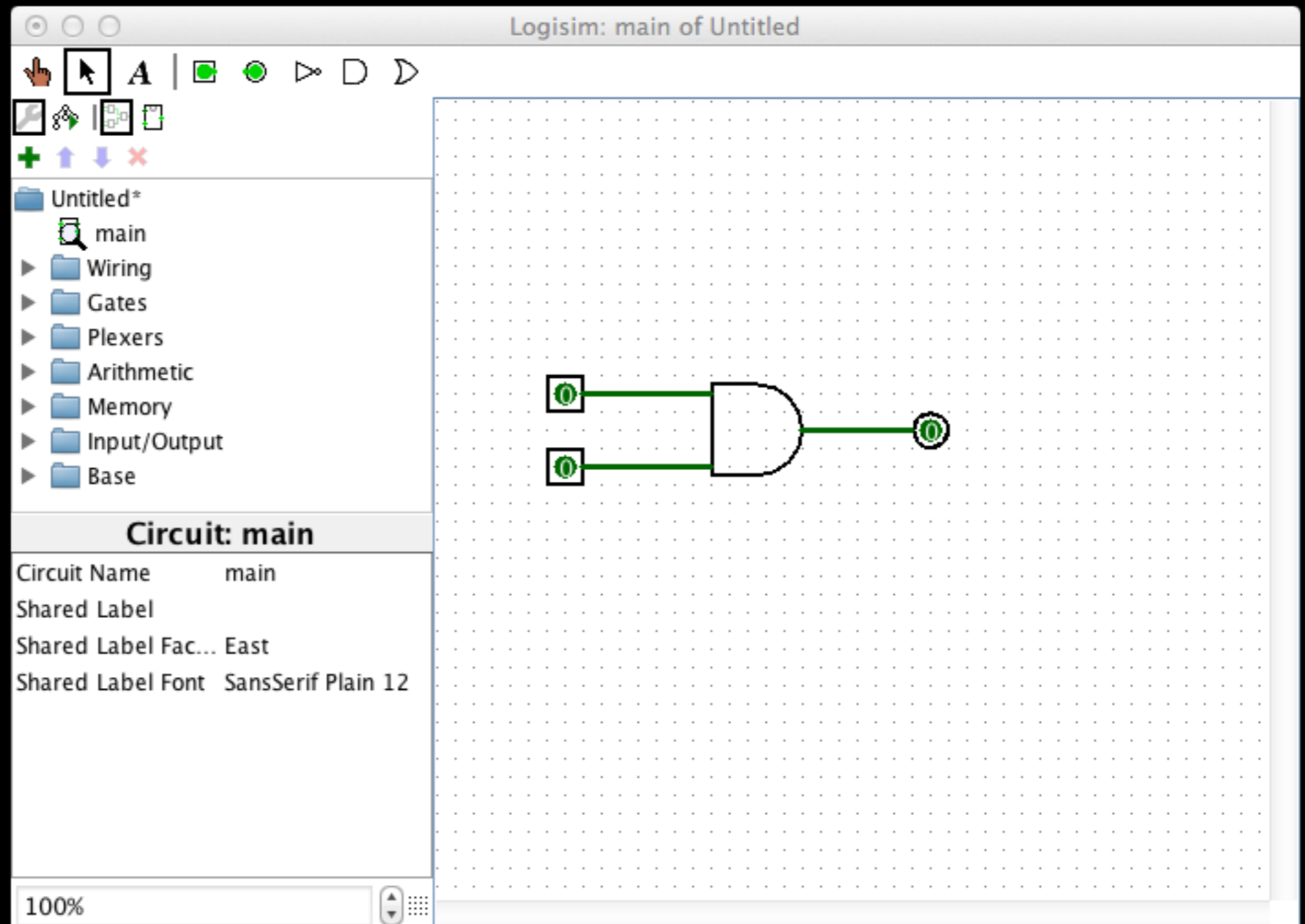
Draw the wires in (click and drag -- if you look closely, you will see little dots where wires can connect)



Use the Poke tool

Use the poke tool to change the values on the input pins

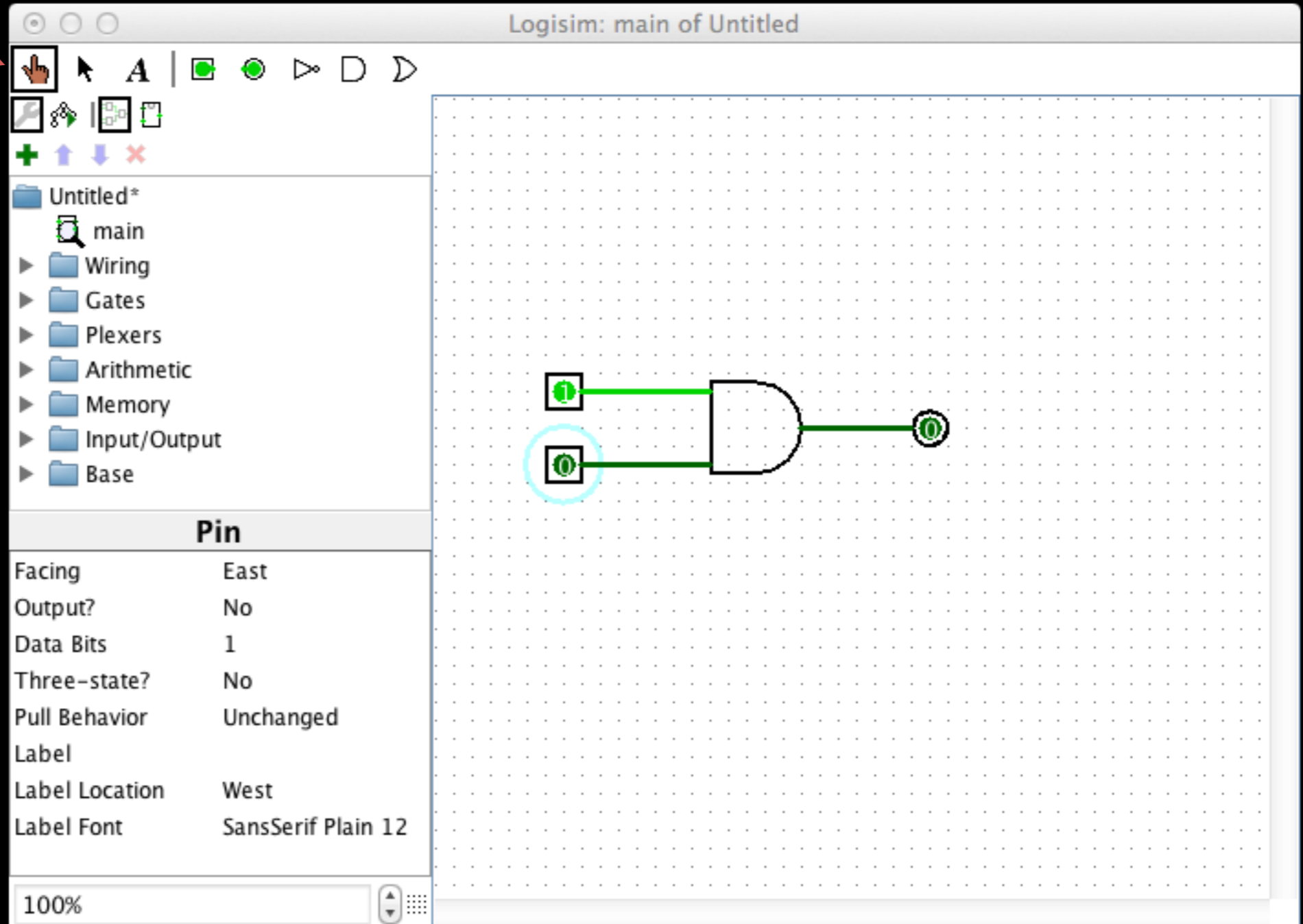Notice that the value changed to a 1 and the wire lit up




The screenshot shows the Logisim software interface. The title bar reads "Logisim: main of Untitled". The top toolbar contains various icons for editing and simulation. The left sidebar shows a project tree with folders for "Wiring", "Gates", "Plexers", "Arithmetic", "Memory", "Input/Output", and "Base". The main workspace displays a circuit on a grid. It features an AND gate with two input pins on the left and one output pin on the right. The top input pin has a value of 1, and the bottom input pin has a value of 0. The output pin has a value of 0. The wire connecting the two input pins to the AND gate is lit up. A red circle highlights the bottom input pin, and another red circle highlights the output pin. The bottom status bar shows "100%" zoom.

Pin	
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

Playing with AND

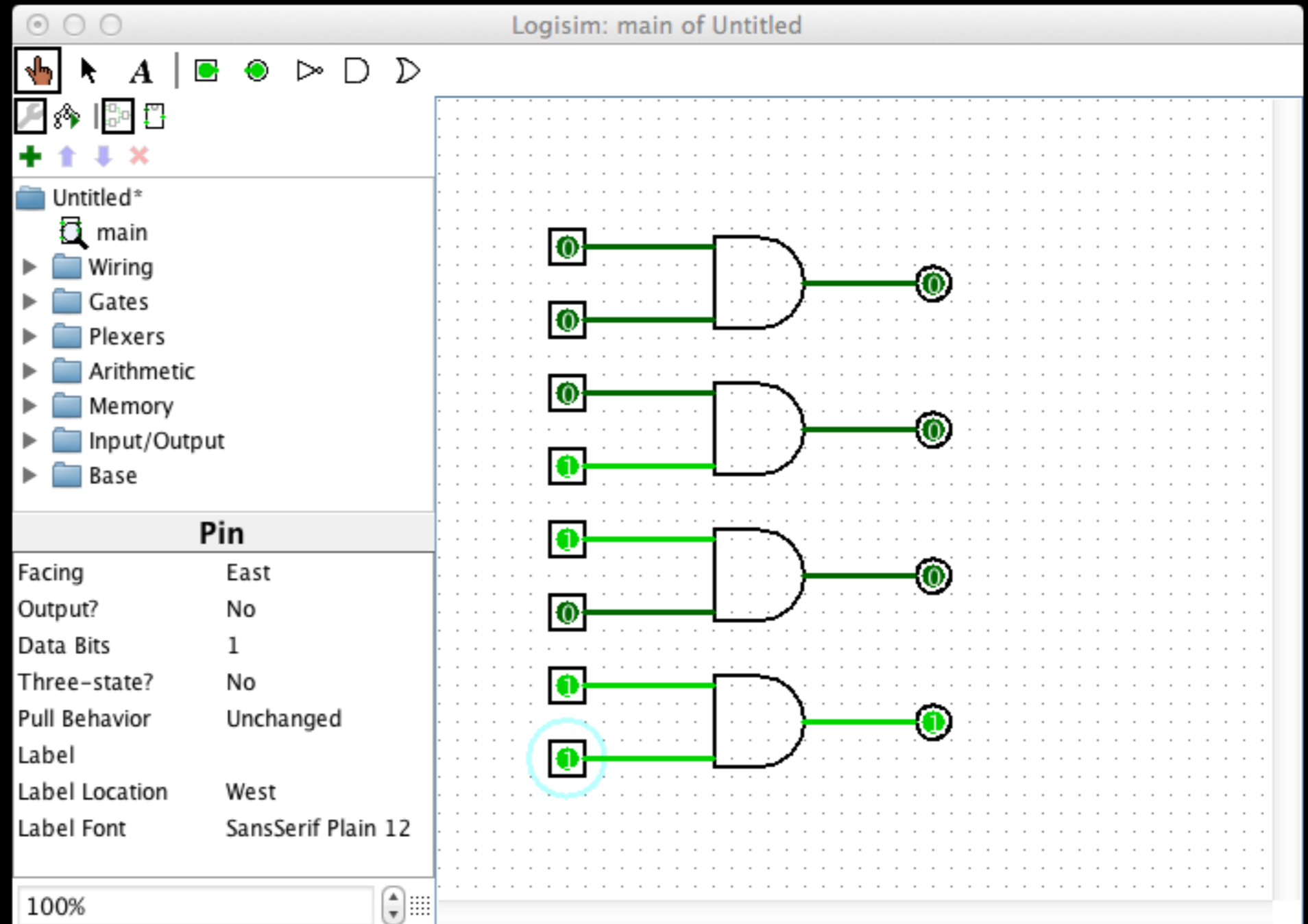Here are the four possible combinations of our two inputs.



The screenshot shows the Logisim software interface. The main workspace contains four AND gates arranged vertically. Each gate has two input pins on the left and one output pin on the right. The input pins are labeled with binary values: 0, 0, 1, 0, 1, 0, 1, 1. The output pins are labeled with binary values: 0, 0, 0, 0, 0, 0, 0, 1. The bottom-most gate, where both inputs are 1 and the output is 1, is highlighted with a blue circle. The left sidebar shows a file explorer with folders for Wiring, Gates, Plexers, Arithmetic, Memory, Input/Output, and Base. Below the file explorer is a 'Pin' configuration table.

Pin	
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

100%

Adding two 1 bit numbers


We would like to build a circuit that can add two 1-bit numbers together

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$
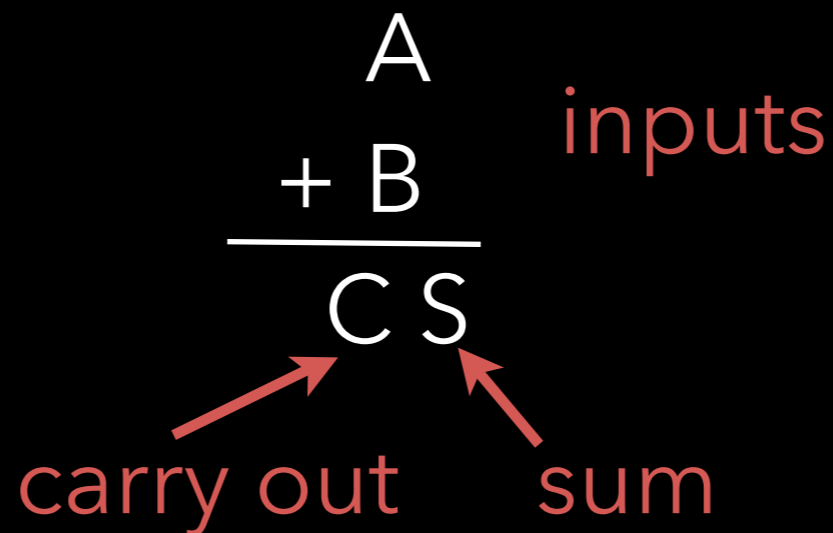
$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$



Build a truth table

We can express this as a **truth table**

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{array}{r} A \\ + B \\ \hline CS \end{array}$$

Convert to equations

Now, we can extract the minterms and write two equations, one for each output

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \bar{A}B + A\bar{B}$$

$$C = AB$$

Equation to gates

We will need two circuits to implement our two equations


$$S = \bar{A}B + A\bar{B}$$

$$C = AB$$


2 AND gates,
1 OR gate and
2 NOT gates

... or 1 XOR

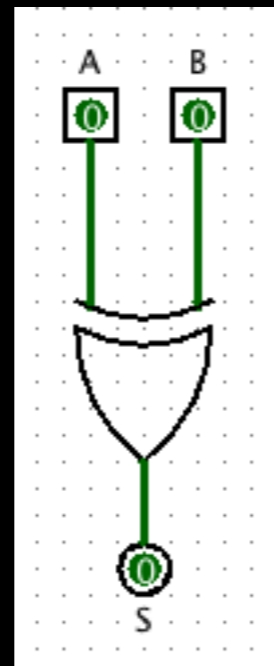XOR stands for exclusive OR. It is true when exactly one of the inputs is true.



1 AND gate

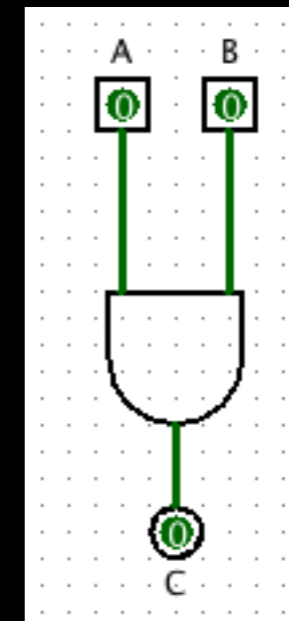

Build the circuit in Logisim


Create a circuit called half_adder
click the green plus sign

click here

new circuit
will show
up here


Make sure that you are
now in the circuit -- it
should have a
magnifying glass on it

Double click to
change circuits

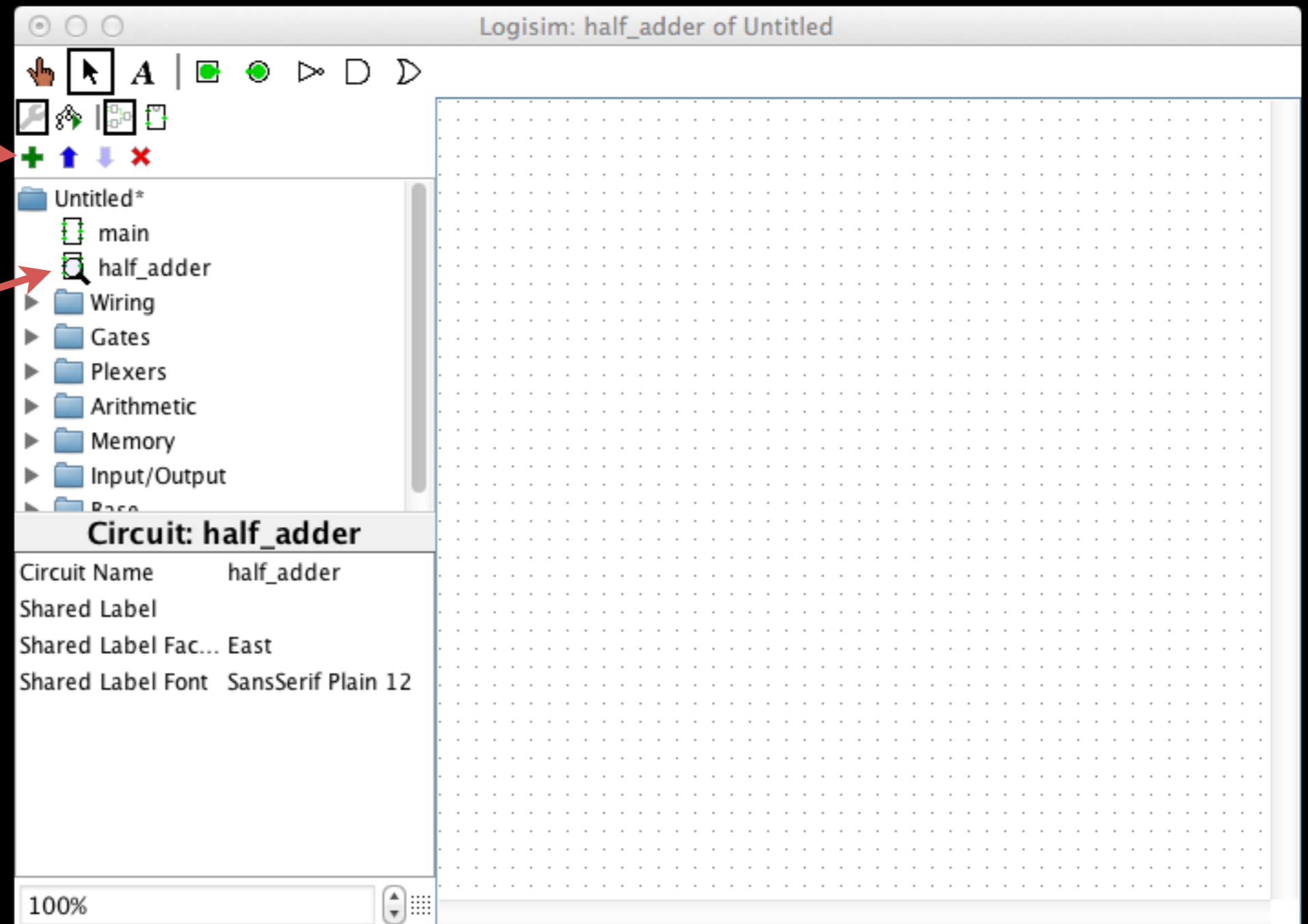

Put together the circuit


The XOR gate is hiding in here

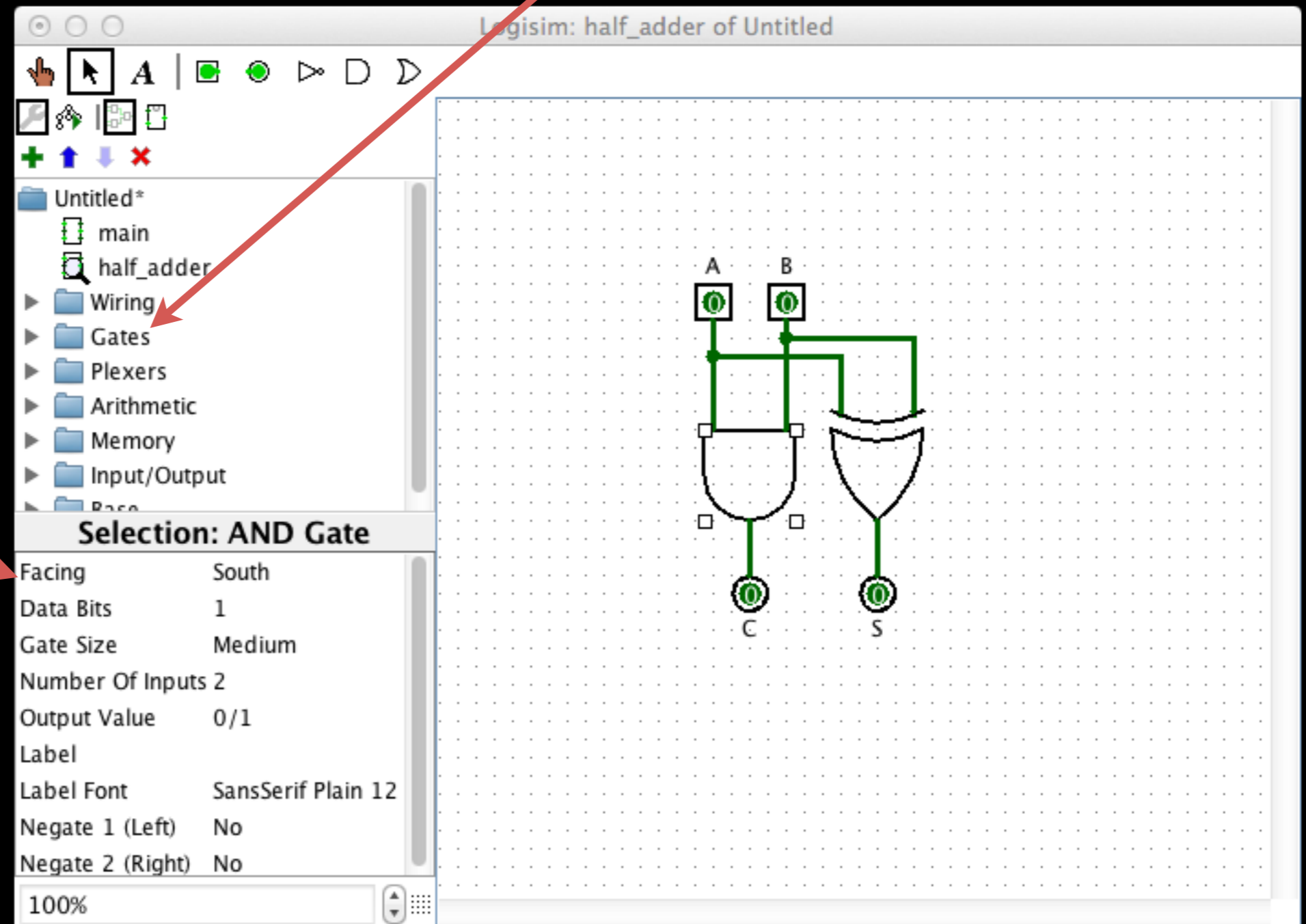

To change the orientation and add labels to the pins, use the attribute panel

Build the circuit in Logisim

Make sure to test your circuit

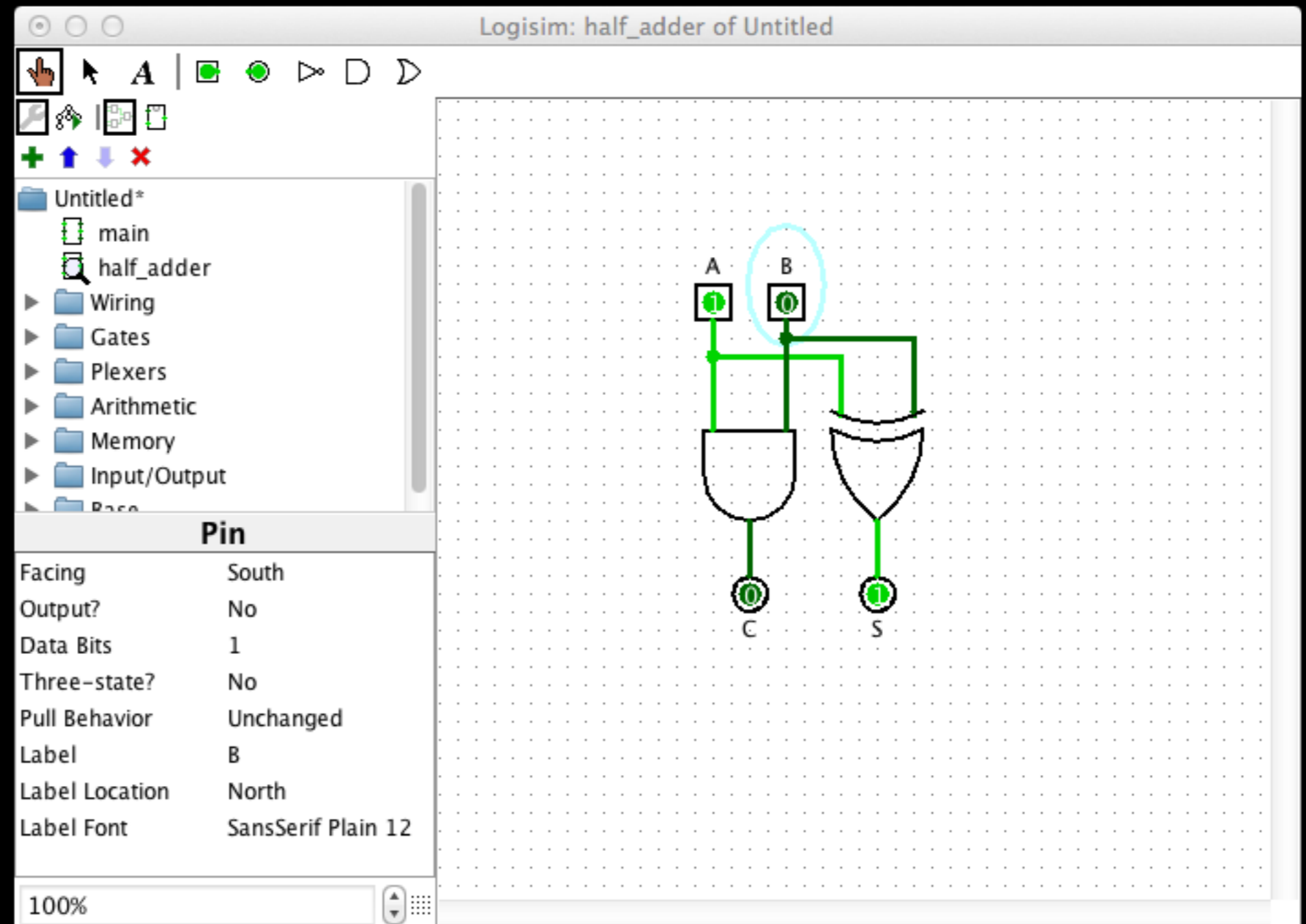

What if the numbers have more than 1 bit?

If we add another bit to each, we have four times the number of possible equations

$$\begin{array}{r} 01 \\ + 01 \\ \hline 010 \end{array} \quad \begin{array}{r} 01 \\ + 00 \\ \hline 001 \end{array} \quad \begin{array}{r} 00 \\ + 01 \\ \hline 001 \end{array} \quad \begin{array}{r} 00 \\ + 00 \\ \hline 000 \end{array} \quad \begin{array}{r} 11 \\ + 01 \\ \hline 100 \end{array} \quad \begin{array}{r} 11 \\ + 00 \\ \hline 011 \end{array} \quad \begin{array}{r} 10 \\ + 01 \\ \hline 011 \end{array} \quad \begin{array}{r} 10 \\ + 00 \\ \hline 010 \end{array}$$

$$\begin{array}{r} 01 \\ + 11 \\ \hline 100 \end{array} \quad \begin{array}{r} 01 \\ + 10 \\ \hline 011 \end{array} \quad \begin{array}{r} 00 \\ + 11 \\ \hline 011 \end{array} \quad \begin{array}{r} 00 \\ + 10 \\ \hline 010 \end{array} \quad \begin{array}{r} 11 \\ + 11 \\ \hline 110 \end{array} \quad \begin{array}{r} 11 \\ + 10 \\ \hline 101 \end{array} \quad \begin{array}{r} 10 \\ + 11 \\ \hline 101 \end{array} \quad \begin{array}{r} 10 \\ + 10 \\ \hline 100 \end{array}$$

Looking at the second column

The second column is not the same -- it has to add three numbers instead of two

$$\begin{array}{r} 1 \\ 11 \\ + 11 \\ \hline 110 \end{array}$$

just looking at the
second column

$$\begin{array}{r} 1 \\ 1 \\ + 1 \\ \hline 11 \end{array}$$


addition is
associative

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \\ + 1 \\ \hline 11 \end{array}$$

... and we already know how to
add two 1 bit numbers together

Making a full adder

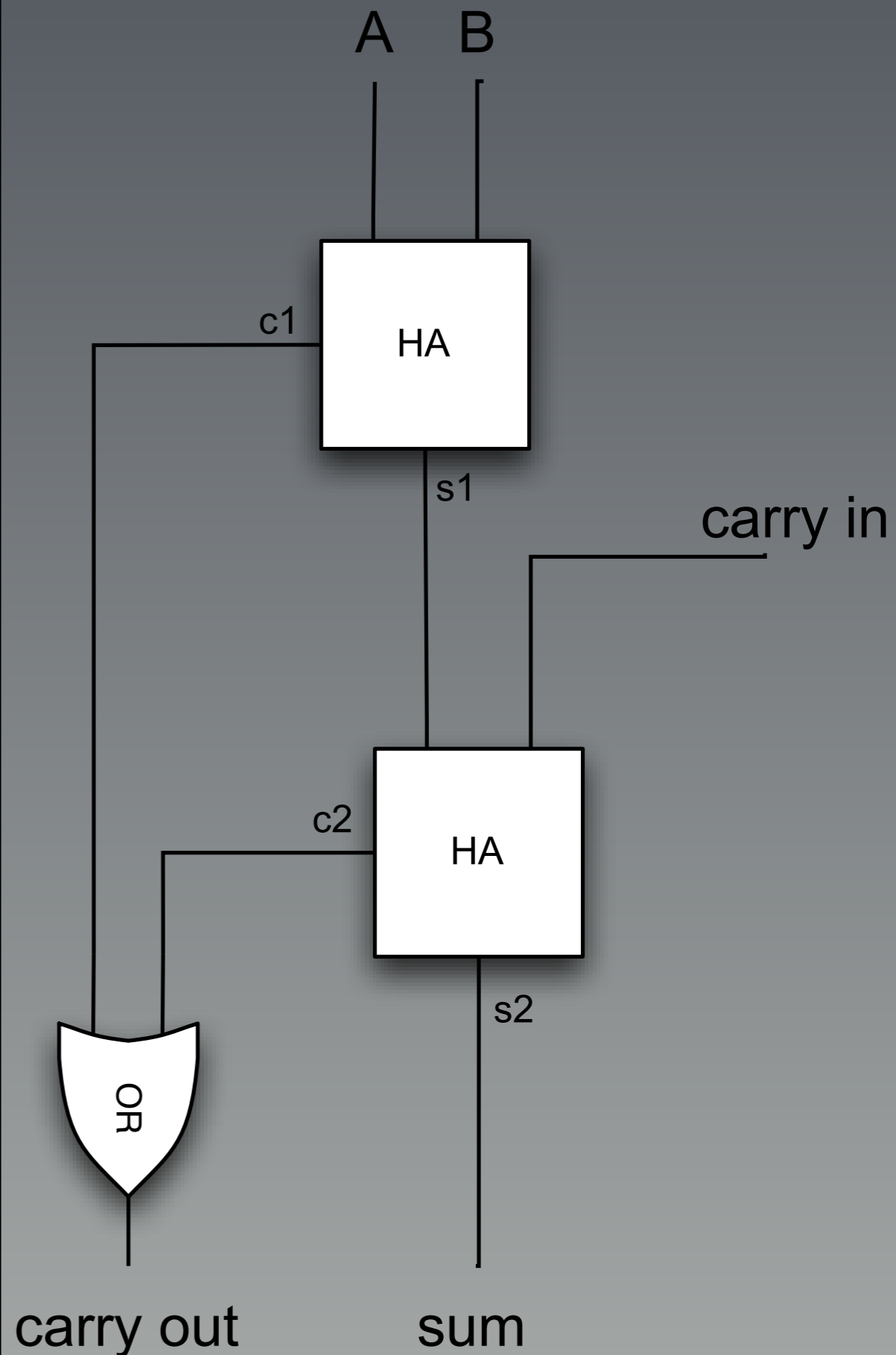The Carry_out is just the OR of the two carries from the half adders because it will never be the case that both half adders produce one (check it yourself)



Make a full adder in Logisim


Create a new circuit and call it full_adder

Add two half_adders to the circuit

just click the half_adder once like it was a gate and then click in your workspace

Add an OR gate


Hook it all together

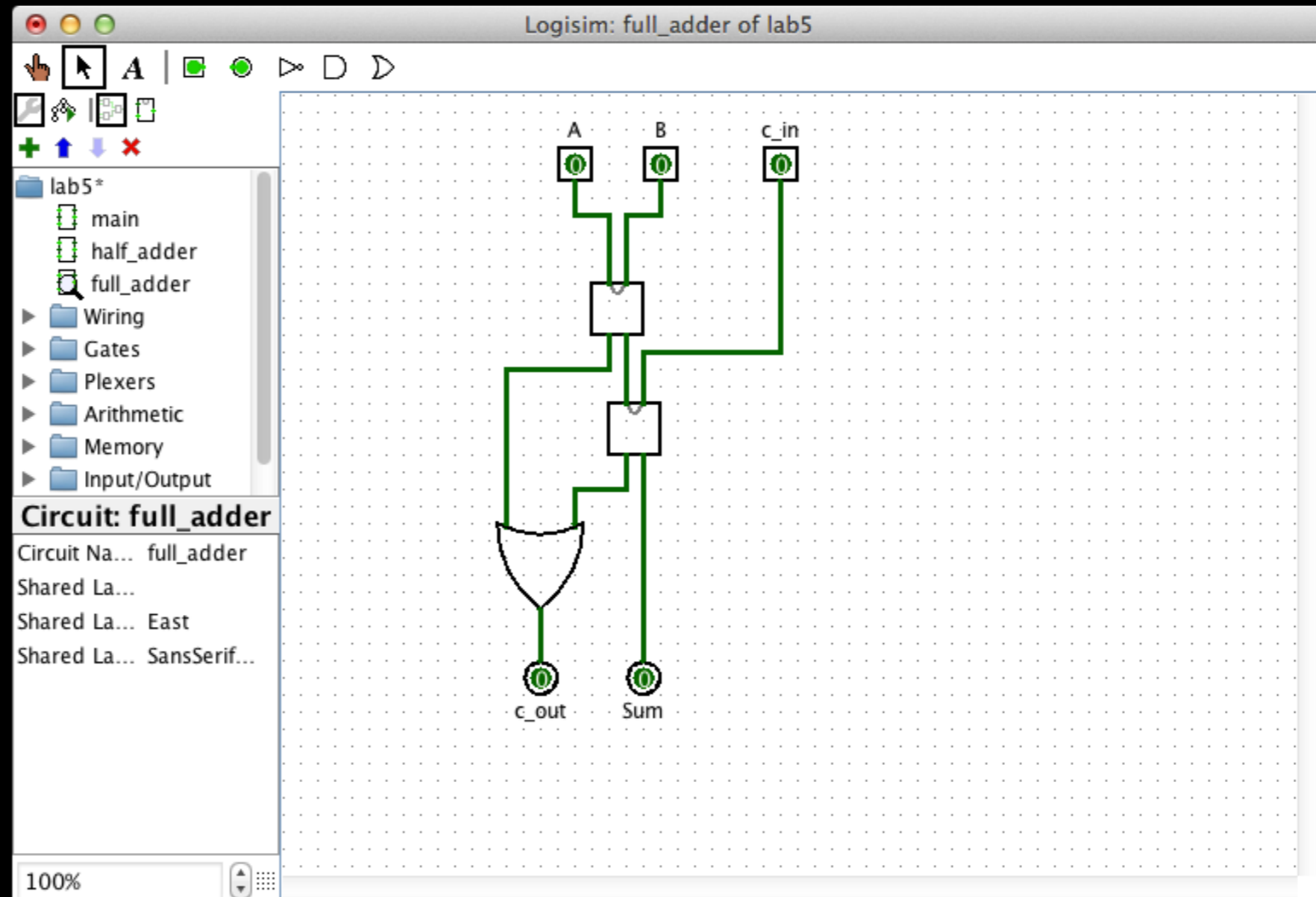

Putting it all together

With a half adder and a couple of full adders, we can make something called **ripple-carry adder**

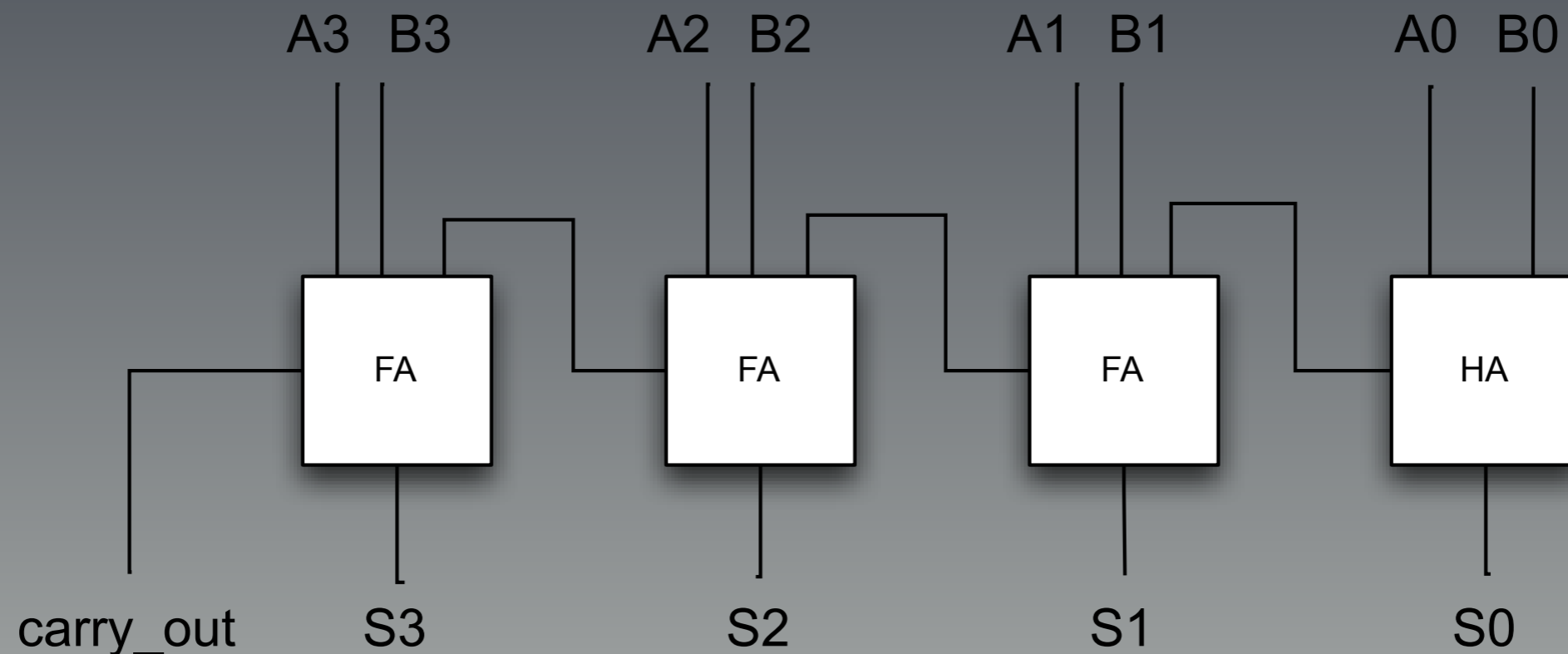called that because any carries generated in the first column can ripple up to the last one



Build a 4-bit adder

- Double click on the main circuit
- Recreate the 4-bit adder from the previous page using three full adders and one half adder
- Add the 8 input pins and five output pins and label them $A_0, A_1, A_2, A_3, B_0, B_1, B_2, B_3, S_0, S_1, S_2, S_3, \text{carry_out}$
 - [note - the wires may not connect in exactly the same place as shown in the diagram]
- Test, test, test